

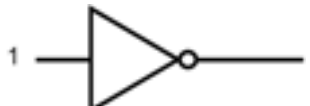





**Question 1**
**6 marks**

Column A Logic gate with input(s)	Column B Output
	1
	0
	0
	1
	0
	0

Each correct response 1 mark