

### Question 1

Logic gates have one or more inputs and a single output. For each logic gate in Column A in the table below enter the output, either 0 or 1, in Column B.

Column A Logic gate with input(s)	Column B Output (0 or 1)
	
	
	
	
	
	